

**CS 223**

**Digital Design**

**Section 01**

**Laboratory Assignment 4**


**Traffic Light System**

**Arda Önal**

**21903350**

**28.11.2020**

a)

 

Moore state machine transition diagram

state	encoding $s_{1:0}$
S0	000
S1	001
S2	010
S3	011
S4	100
S5	101
S6	110
S7	111

State encodings

Output	Encoding $L_{2:0}$
green	011
yellow	001
red	111

Output encodings

current state			inputs		next state		
$s_2$	$s_1$	$s_0$	$s_a$	$s_b$	$s'_2$	$s'_1$	$s'_0$
0	0	0	0	X	0	0	1
0	0	0	1	X	0	0	0
0	0	1	X	X	0	1	0
0	1	0	X	X	0	1	1
0	1	1	X	X	1	0	0
1	0	0	X	1	1	0	0
1	0	0	X	0	1	0	1
1	0	1	X	X	1	1	0
1	1	0	X	X	1	1	1
1	1	1	X	X	0	0	0

**State transition table**

**Next state equations:**

$$S'_2 = \bar{S}_2 S_1 S_0 + S_2(\bar{S}_1 + \bar{S}_0)$$

$$S'_1 = S_1 \oplus S_0$$

$$S'_0 = \bar{S}_0 (S_1 + \bar{S}_2 \bar{S}_A + S_2 \bar{S}_B)$$

current state			outputs					
s <sub>2</sub>	s <sub>1</sub>	s <sub>0</sub>	L <sub>a2</sub>	L <sub>a1</sub>	L <sub>a0</sub>	L <sub>b2</sub>	L <sub>b1</sub>	L <sub>b0</sub>
0	0	0	0	1	1	1	1	1
0	0	1	0	0	1	1	1	1
0	1	0	1	1	1	1	1	1
0	1	1	1	1	1	0	0	1
1	0	0	1	1	1	0	1	1
1	0	1	1	1	1	0	0	1
1	1	0	1	1	1	1	1	1
1	1	1	0	0	1	1	1	1

**Output table**

**Output equations:**

$$L_{a2} = (S_1 \oplus S_2) + S_1 \bar{S}_0$$

$$L_{a1} = (S_1 \oplus S_2) + \bar{S}_0$$


$$L_{a0} = 1$$

$$L_{b2} = (\bar{S}_2 \oplus S_1) + \bar{S}_2 \bar{S}_0$$

$$L_{b1} = (\bar{S}_2 \oplus S_1) + \bar{S}_0$$

$$L_{b0} = 1$$

## Finite State Machine schematic

 

**b)** We need three flip-flops to implement this problem. This because our states have three bit encodings which means that our register will need 3 flip-flops to work.

**c)** We need to count  $15 \times 10^7$  rising edges to obtain 1/3 Hz frequency. This is because BASYS3 has a clock speed of 100MHz and obtaining 1/3 Hz frequency means counting  $3 \times 10^8$  transitions. Since half of these transitions are rising edges, our answer is  $3 \times 10^8 / 2 = 15 \times 10^7$ .

**SystemVerilog code that will count original clock cycles output HIGH in every 3 seconds:**

```
module clock_counter(input clock, input reset, output logic new_clock);
```

```
    localparam risingEdgeNumber = 150000000; // The number we found in partC of lab04
```

```
    logic [31:0] count;
```

```

always @ (posedge(clock), posedge(reset))
begin
    if (reset == 1'b1)
        count <= 32'b0;
    else if (count == risingEdgeNumber - 1)
        count <= 32'b0;
    else
        count <= count + 1;
end

```

```

always @ (posedge(clock), posedge(reset))
begin
    if (reset == 1'b1)
        new_clock <= 1'b0;
    else if (count == risingEdgeNumber - 1)
        new_clock <= ~new_clock;
    else
        new_clock <= new_clock;
end

```

endmodule

**d) SystemVerilog code for the traffic light system:**

```

module traffic_light_system(input logic clk,reset,sa,sb,output logic [2:0] La, Lb);

    typedef enum logic [2:0] {S0, S1, S2, S3, S4, S5, S6, S7} statetype;
    statetype state, nextstate;

    // state register
    always_ff @(posedge clk, posedge reset)
    if (reset) state <= S0;
    else state <= nextstate;

```

```

// next state logic
always_comb
    case (state)
        S0: if (sa) nextstate = S0;
            else nextstate = S1;
        S1: nextstate = S2;
        S2: nextstate = S3;
        S3: nextstate = S4;
        S4: if (sb) nextstate = S4;
            else nextstate = S5;
        S5: nextstate = S6;
        S6: nextstate = S7;
        S7: nextstate = S0;
        default: nextstate = S0;
    endcase

// output logic
logic n0;
logic n1;
xor(n0,state[1],state[2]);
xnor(n1,state[1],state[2]);

assign La[2] = n0 | (state[1] & ~state[0]);
assign La[1] = n0 | ~state[0];
assign La[0] = 1;

assign Lb[2] = n1 | (~state[2] & ~state[0]);
assign Lb[1] = n1 | ~state[0];
assign Lb[0] = 1;
endmodule

```

### **Testbench for the traffic light system:**

```
module testbench_traffic();  
    logic clk,reset,sa,sb;  
    logic [2:0] La, Lb;  
  
    // instantiate device under test  
    traffic_light_system dut(clk,reset,sa,sb,La,Lb);  
  
    // clock  
    always  
        begin  
            clk = 1; #5;  
            clk = 0; #5;  
        end  
  
    // apply inputs one at a time  
    initial begin  
        reset = 1; sa= 1; sb = 0; #10;  
        reset = 0; #100;  
        sb = 1; #100;  
        sa = 0; #100;  
        sa = 0; sb = 0; #100;  
    end  
endmodule
```



**e) SystemVerilog code for combined new clock generator in part c and traffic light system in part d:**

```
module combined_traffic_light(input logic clk,reset,sa,sb,output logic [2:0] La, Lb);  
    logic new_clock;  
    clock_counter newclock(clk,reset,new_clock);  
    traffic_light_system improved_fsm(new_clock,reset,sa,sb,La,Lb);  
endmodule
```