

CS 223

Digital Design

Section 01

Laboratory Assignment 3

Modeling Decoders and MUXs
in System Verilog

Arda Önal

21903350

24.10.2020

b) Behavioral SystemVerilog module for 2-to-4 decoder and a testbench for it.

```
module two_to_four_decoder( input logic a0, a1, output logic y0, y1, y2, y3);

    assign y0 = ~a0 & ~a1;
    assign y1 = a0 & ~a1;
    assign y2 = ~a0 & a1;
    assign y3 = a0 & a1;

endmodule
```

Testbench:

```
module testbench_two_to_four_decoder();

    logic a0, a1;
    logic y0, y1, y2, y3;

    two_to_four_decoder dut( a0, a1, y0, y1, y2, y3);

    initial begin
        a0 = 0; a1 = 0; #10;
        if ( y0 != 1 | y1 != 0 | y2 != 0 | y3 != 0) $display("00 failed.");
        a0 = 1; #10;
        if ( y0 != 0 | y1 != 1 | y2 != 0 | y3 != 0) $display("10 failed.");
        a0 = 0; a1 = 1; #10;
        if ( y0 != 0 | y1 != 0 | y2 != 1 | y3 != 0) $display("01 failed.");
        a0 = 1; #10;
        if ( y0 != 0 | y1 != 0 | y2 != 0 | y3 != 1) $display("11 failed.");
    end

endmodule
```

c) Behavioral SystemVerilog module for 4-to-1 multiplexer.

```
module four_to_one_mux(input logic [3:0]d,[1:0]s, output logic y);
```

```
    assign y = s[1] ? (s[0] ? d[3] : d[2]) : ( s[0] ? d[1] : d[0]);
```

```
endmodule
```

Testbench:

```
module testbench_four_to_one_mux();
```

```
    logic [3:0]d;
```

```
    logic [1:0]s;
```

```
    logic y;
```

```
    four_to_one_mux dut(d,s,y);
```

```
    initial begin
```

```
        for ( int i = 0; i < 64; i++) begin
```

```
            {d, s} = i; #9;
```


```
            if ( y != d[s]) $display( "%0d failed", {d,s});
```

```
        end
```

```
    end
```

```
endmodule
```

 d) Schematic (block diagram) and structural System Verilog module of 8-to-1 MUX by using two 4-to-1 MUX modules, two AND gates, an INVERTER, and an OR gate. Prepare a test bench for it.



Structural System Verilog module of 8-to-1 MUX by using two 4-to-1 MUX modules:

```
module eight_to_one_mux(input logic [7:0]d,[2:0]s, output logic y);
```

```
    logic mux0;
```

```
    logic mux1;
```

```
    logic node0;
```

```
    logic node1;
```

```
    four_to_one_mux multiplexer0( d[3:0], s[1:0], mux0);
```


```
    four_to_one_mux multiplexer1( d[7:4], s[1:0], mux1);
```

```
    and( node0, ~s[2], mux0);  
    and( node1, s[2], mux1);  
    or( y, node0, node1);  
endmodule
```

Testbench:

```
module testbench_eight_to_one_mux();  
  
    logic [7:0]d;  
    logic [2:0]s;  
    logic y;  
  
    eight_to_one_mux mux8(d[7:0],s[2:0],y);  
  
    initial begin  
        for ( int i = 'd0; i < 'd2048; i++) begin  
            {d,s} = i; #0.3;  
            if ( y != d[s]) $display( "%0d failed", {d,s});  
        end  
    end  
endmodule
```

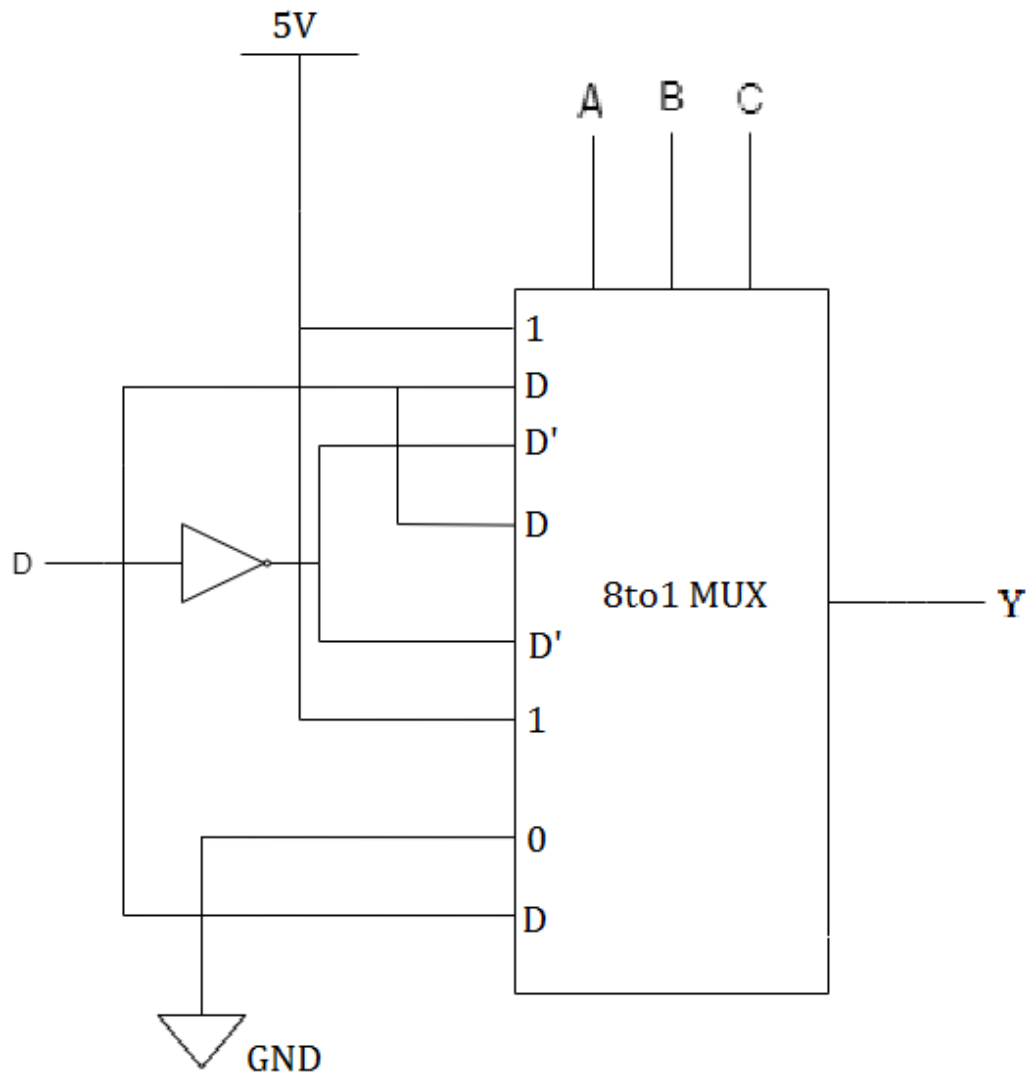e) Schematic (block diagram) and SystemVerilog module for $F(A,B,C,D)=\sum(0,1,3,4,7,8,10,11,15)$ function, using one (not two) 8-to-1 multiplexer and an inverter.



```

module functionF(input logic a,b,c,d, output logic y);
    logic dnot;
    not inverter(dnot,d);

    eight_to_one_mux mux8({d, 1'b0, 1'b1, dnot, d, dnot, d, 1'b1}, {a, b, c}, y);
endmodule

```

```
module partE_testbench();  
    logic a,b,c,d;  
    logic y;  
  
    functionF dut( a,b,c,d, y);  
  
    initial begin  
  
        for ( int i = 0; i < 16; i++) begin  
            {a,b,c,d} = i; #10;  
        end  
    end  
endmodule
```